

## Cascading of Amplifier :

The block diagram of a Cascade amplifier is shown in Fig-1

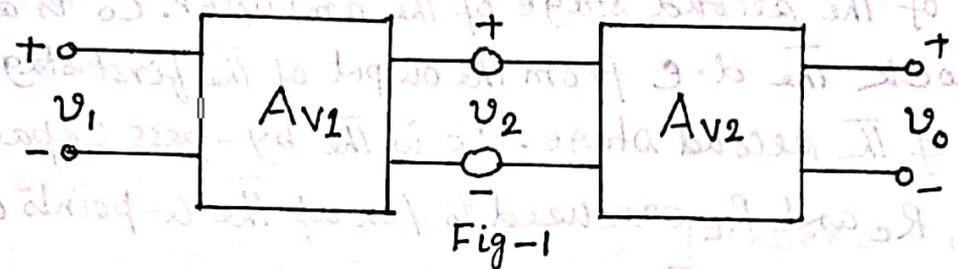


Fig-1

The effective voltage gain of the Cascade amplifier is given by

$$A_v = A_{v1} \times A_{v2} \dots \dots \dots (1)$$

Thus in cascading, we increase the voltage gain. But Common Collector amplifiers are not cascaded because their voltage gain is less than unity. Only CE amplifiers are cascaded.

## R-C Coupled Transistor Amplifier :

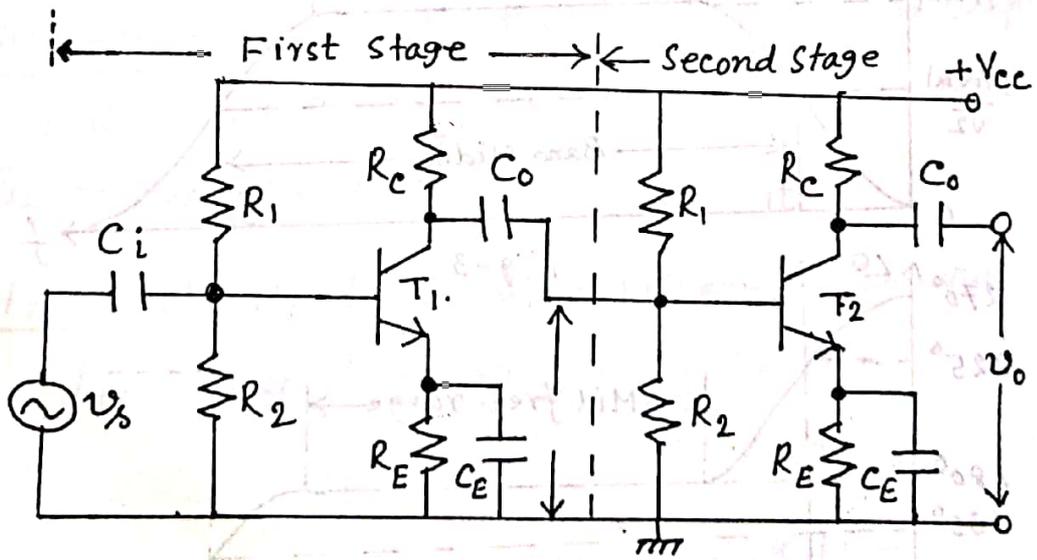


Fig-2



8.

A two stage R-C Coupled transistor amplifier in CE mode Connection is shown in Fig-2.  $C_o$  is the coupling capacitor which couples the output voltage  $v_2$  of the first stage to the input of the second stage of the amplifier.  $C_o$  is also used to block the d.c from the output of the first stage to the input of the second stage.  $C_E$  is the by-pass capacitor.  $R_1, R_2, R_c$  and  $R_E$  are used to fix up the Q-points of the transistors  $T_1$  and  $T_2$

The voltage gain of the first stage of the R-C Coupled amplifier is given by

$$A_v = \frac{v_2}{v_s} = |A_v| \angle \theta \text{ --- (2)}$$

The variations of  $|A_v|$  and  $\angle \theta$  with frequency  $f$  are shown in Fig-3 and Fig-4.

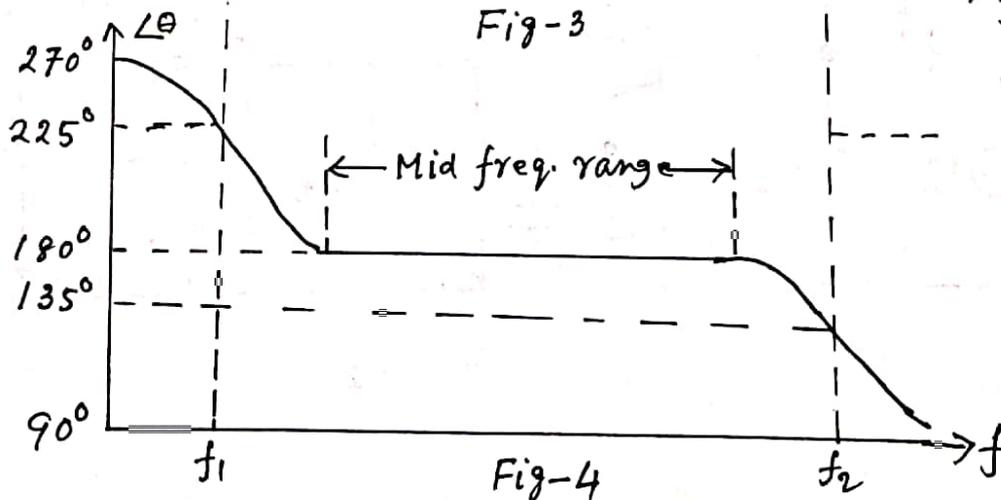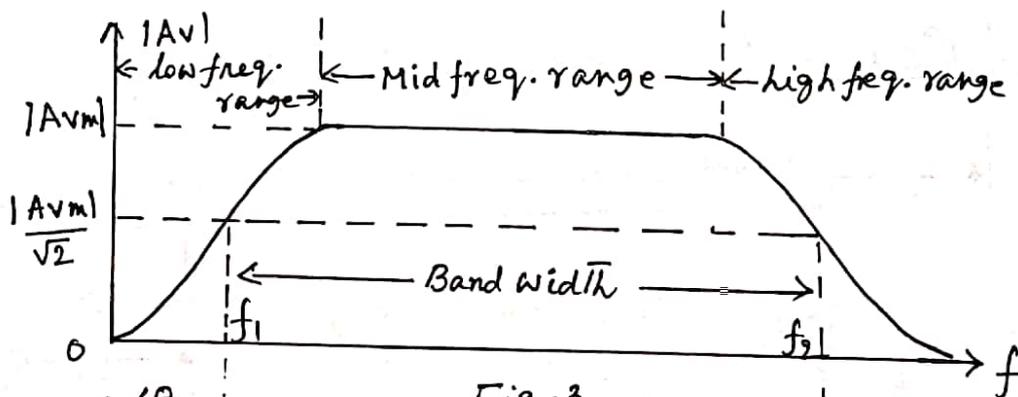

### The decibel (dB):-

The telephone industries generally use a unit based on logarithms to the base 10, naming the unit bel for Alexander Graham Bell. The bel is defined as the logarithm of a power ratio i.e. power gain

$$\text{No. of bels} = \log_{10} \left( \frac{P_2}{P_1} \right)$$

where  $P_2$  = output power and  $P_1$  = input power of a circuit. The decibel denoted by dB, is defined by the relation

$$\text{dB} = 10 \log_{10} \left( \frac{P_2}{P_1} \right)$$

For the case of equal resistances at the input and output circuits

$$\text{dB} = 10 \log_{10} \left( \frac{v_2}{v_1} \right)^2 = 20 \log_{10} \left( \frac{v_2}{v_1} \right) = 20 \log_{10} \left( \frac{I_2}{I_1} \right)$$

**Problem 1**: The output voltage of an amplifier is 10V at 5 KHz and 7.07V at 25 KHz. What is the decibel change in the output power level?

Sol<sup>n</sup>: Let  $v_1$  be the input voltage (standard voltage)

In first case the power gain at 5 KHz is

$$\text{dB} = 20 \log_{10} \left( \frac{10}{v_1} \right)$$

In second case, power gain at 25 KHz is

$$\text{dB} = 20 \log_{10} \left( \frac{7.07}{v_1} \right)$$

Therefore decibel change in power level

$$\begin{aligned}
 &= 20 \log_{10} \left( \frac{7.07}{v_1} \right) - 20 \log_{10} \left( \frac{10}{v_1} \right) \\
 &= 20 \left[ \log_{10} 7.07 - \log_{10} v_1 - \log_{10} 10 + \log_{10} v_1 \right] \\
 &= 20 \log_{10} \left( \frac{7.07}{10} \right) = 20 \log_{10} (0.707) \\
 &= -3 \text{ dB.}
 \end{aligned}$$

### Frequency Response of R-C Coupled Amplifier :


The variation of voltage gain  $|A_v|$  of an amplifier with frequency of input signal is shown in fig-3. The gain remains practically constant over a wide range of frequencies in the 'mid frequency range', but the gain decreases both in the low frequency range with decrease in frequency and in the high frequency range with increase in frequency. The frequency response is determined by the coupling capacitor  $C_o$  and various transistor junction capacitances. We calculate the voltage gain in different frequency ranges.

### Mid-Frequency Range :

The reactances offered by  $C_o$  and  $C_E$  are so small that they are a.c short circuited. The junction capacitances

are so small that their reactances are very large. As they appear effectively in parallel with the associated resistances these reactances need not be considered in the mid-frequency range.

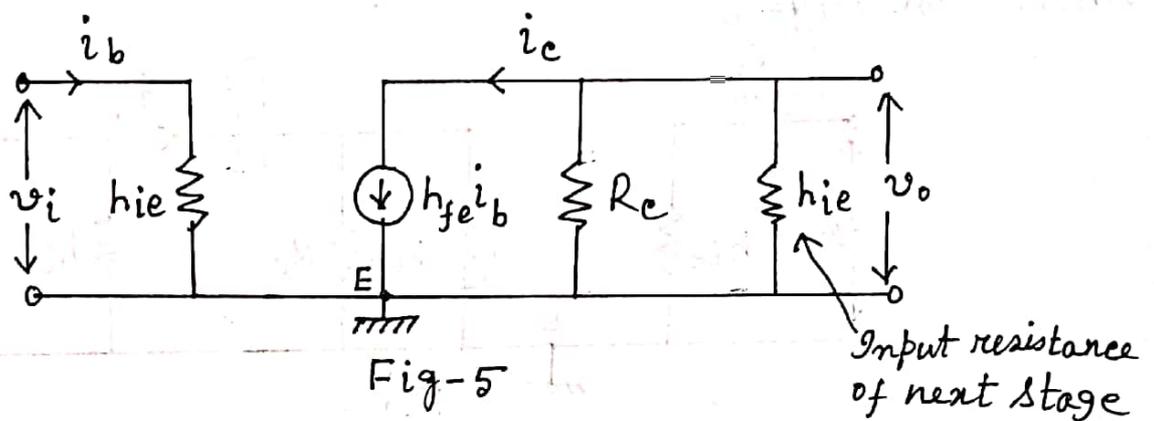The approximate h-parameter equivalent circuit including input resistance of the next stage is shown in Fig-5. We assume the transistors are identical and  $R_1$  and  $R_2$  are large enough.



The output voltage

$$v_o = -h_{fe} i_b \cdot (R_c \parallel h_{ie})$$

$$= -h_{fe} i_b \cdot \frac{R_c h_{ie}}{R_c + h_{ie}} \quad \text{--- (1)}$$

The input voltage

$$v_i = h_{ie} i_b \quad \text{--- (2)}$$

Therefore the voltage gain in mid-frequency range

$$A_{VM} = \frac{v_o}{v_i} = - \frac{h_{fe} R_c}{R_c + h_{ie}} \quad \text{--- (3)}$$

$A_{VM}$  is independent of the frequency of the input signal.

## Low Frequency Range :-

In the low frequency range, the effect of various junction capacitors and  $C_E$  (by-pass capacitor) remains negligible while the reactance of  $C_o$  (Coupling capacitor) becomes appreciable. The a.c drop across  $C_o$  causes reduction of voltage gain. The approximate h-parameter a.c equivalent circuit in the low frequency range is shown in Fig-6

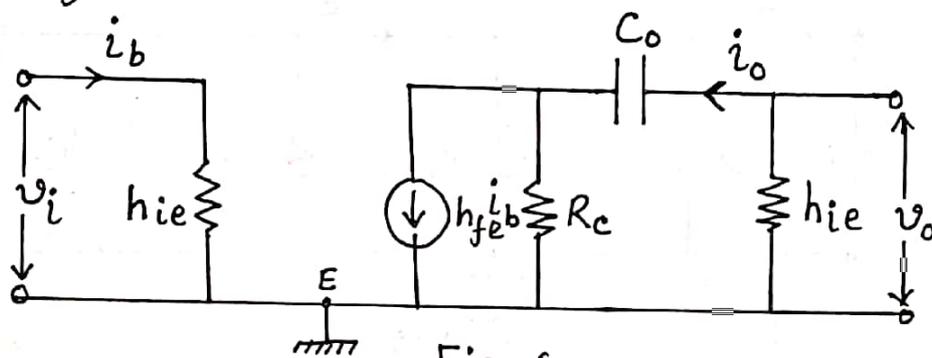


Fig-6

It is assumed that the transistors are identical and  $R_1 \parallel R_2 \gg h_{ie}$ . The output voltage is

$$v_o = -i_o h_{ie} = - \frac{(h_{fe} i_b) R_c}{R_c + h_{ie} + \frac{1}{j\omega C_o}} \cdot h_{ie} \quad \text{--- (4)}$$

$$\text{The input voltage } v_i = h_{ie} i_b \quad \text{--- (5)}$$

Therefore the voltage gain at low frequency range

$$\begin{aligned} A_{vL} &= \frac{v_o}{v_i} = - \frac{h_{fe} R_c}{h_{ie} + R_c - \frac{j}{\omega C_o}} \\ &= - \frac{h_{fe} R_c}{(h_{ie} + R_c) \left[ 1 - \frac{j}{\omega C_o (h_{ie} + R_c)} \right]} \end{aligned}$$

$$\Rightarrow A_{vL} = - \frac{\left( \frac{h_{fe} R_c}{h_{ie} + R_c} \right)}{1 - \frac{j}{\omega C_o (h_{ie} + R_c)}}$$

$$\Rightarrow A_{vL} = \frac{A_{vM}}{1 - j \left( \frac{\omega_1}{\omega} \right)} = \frac{A_{vM}}{1 - j \left( \frac{2\pi f_1}{2\pi f} \right)} \quad [\text{using (3)}]$$

$$\therefore A_{vL} = \frac{A_{vM}}{1 - j \left( \frac{f_1}{f} \right)} \quad \text{--- (6)}$$

$$\text{where } \omega_1 = \frac{1}{C_o (h_{ie} + R_c)}$$

$$\therefore f_1 = \frac{1}{2\pi C_o (h_{ie} + R_c)} \quad \text{--- (7)}$$

and  $f_1 = \frac{\omega}{2\pi}$  is the frequency of the input signal.

From (6) we can write


$$\left| \frac{A_{vL}}{A_{vM}} \right| = \frac{1}{\sqrt{1 + \left( \frac{f_1}{f} \right)^2}} \quad \text{--- (8)}$$

Equation (8) clearly shows that the voltage gain of the amplifier at low frequency range decreases with decrease in the frequency of the input signal. At  $f = f_1$ ,  $|A_{vL}| = \frac{1}{\sqrt{2}} |A_{vM}|$  and the power delivered to the load is reduced by a factor  $\frac{1}{2}$ . For this  $f_1$  is called lower half power frequency or lower 3dB frequency.

14.
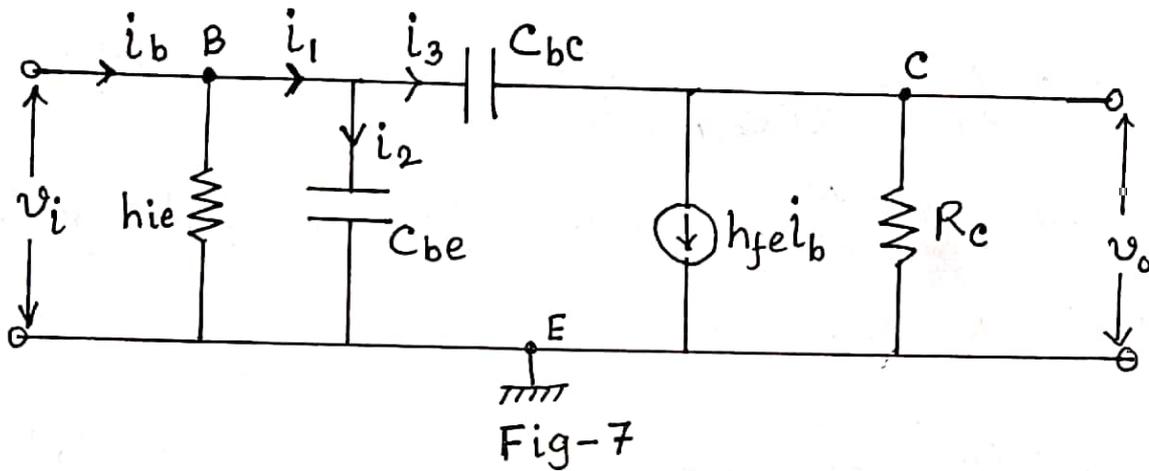
### High Frequency Range:-

At high frequencies The capacitors  $C_o$  and  $C_E$  may be assumed to be virtually a.c short circuited and Their effects are neglected. But The effect of  $C_{be}$  and  $C_{bc}$  Can not be neglected as They tend to shunt The load resistance. The effective a.c load becomes smaller and hence The voltage gain decreases with increase of frequency. The approximate h-parameter a.c equivalent circuit for high frequency range is shown in Fig-7.



From This Fig-7 we can write

$$\begin{aligned}
 i_1 &= i_2 + i_3 = \frac{v_i}{\frac{1}{j\omega C_{be}}} + \frac{v_i - v_o}{\frac{1}{j\omega C_{bc}}} \\
 &= j\omega C_{be} v_i + j\omega C_{bc} v_i \left(1 - \frac{v_o}{v_i}\right) \\
 &= j\omega v_i \left[ C_{be} + C_{bc} \left(1 - \frac{v_o}{v_i}\right) \right] \quad \dots (9)
 \end{aligned}$$

Now using the approximate relation

$$\frac{v_o}{v_i} \approx - \frac{h_{fe} R_c}{h_{ie}}, \text{ the equation (9) becomes}$$

$$i_1 = v_i j\omega \left[ C_{be} + \left( 1 + \frac{h_{fe} R_c}{h_{ie}} \right) C_{bc} \right]$$

$$\Rightarrow i_1 = \frac{v_i}{\frac{1}{j\omega C_d}} = \frac{v_i}{j\omega C_d} \quad \text{--- (10)}$$

$$\text{where } C_d = C_{be} + \left( 1 + \frac{h_{fe} R_c}{h_{ie}} \right) C_{bc} \quad \text{--- (11)}$$

The eq<sup>n</sup> (10) indicates that  $C_{be}$  and  $C_{bc}$  are in effect equivalent to a single capacitor  $C_d$  connected across the input resistance  $h_{ie}$ . The eq<sup>n</sup> (11) shows that base-collector junction capacitor  $C_{bc}$  which provides feedback from output to the input, has the effect of a larger capacitance at the input. This amplification of capacitance is known as Miller effect.

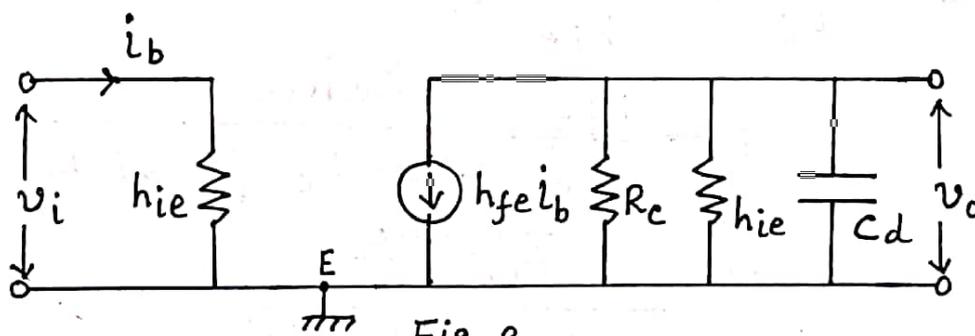


Fig-8

We assume  $R_1 \parallel R_2 \gg h_{ie}$ . The h-parameter a-c equivalent circuit is shown in Fig-8

Now The input voltage

$$v_i = h_{ie} i_b \quad \text{--- (12)}$$

The output voltage

$$v_o = -h_{fe} i_b \cdot Z \quad \text{--- (13)}$$

where

$$\frac{1}{Z} = \frac{1}{R_c} + \frac{1}{h_{ie}} + \frac{1}{\frac{1}{j\omega C_d}}$$

$$= \frac{1}{R_c} + \frac{1}{h_{ie}} + j\omega C_d$$

$$= \frac{h_{ie} + R_c + j\omega C_d R_c h_{ie}}{R_c h_{ie}}$$

$$\therefore Z = \frac{R_c h_{ie}}{h_{ie} + R_c + j\omega C_d R_c h_{ie}}$$

Hence The high frequency voltage gain

$$A_{vH} = \frac{v_o}{v_i} = - \frac{h_{fe}}{h_{ie}} \cdot Z$$

$$= - \frac{h_{fe}}{h_{ie}} \cdot \frac{R_c h_{ie}}{h_{ie} + R_c + j\omega C_d R_c h_{ie}}$$

$$= \frac{-h_{fe} R_c}{(h_{ie} + R_c)} \cdot \frac{1}{1 + j\omega \left( \frac{C_d R_c h_{ie}}{h_{ie} + R_c} \right)}$$

$$\therefore A_{vH} = \frac{A_{vM}}{1 + j\left(\frac{\omega}{\omega_2}\right)} = \frac{A_{vM}}{1 + j\left(\frac{f}{f_2}\right)} \quad \text{--- (14)}$$

$$\text{Where } \frac{1}{\omega_2} = \frac{C_d R_{c h i e}}{h_{i e} + R_c}$$

$$\Rightarrow \omega_2 = \frac{h_{i e} + R_c}{C_d (h_{i e} R_c)}$$

$$\therefore f_2 = \frac{1}{2\pi C_d} \cdot \left( \frac{h_{i e} + R_c}{h_{i e} R_c} \right) \quad \text{--- (15)}$$

From (14)

$$\left| \frac{A_{vH}}{A_{vM}} \right| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_2}\right)^2}} \quad \text{--- (16)}$$

The equation (16) shows that the voltage gain decreases in the high frequency range with increase in the frequency  $f$  of the input signal. At  $f = f_2$ ; the voltage gain  $|A_{vH}|$  reduces to  $\frac{1}{\sqrt{2}}$  of its mid-frequency value and the power is reduced by a factor of  $\frac{1}{2}$ . For this  $f_2$  is called upper half power frequency or upper 3 dB frequency.

Bandwidth (B.W) and Gain-B.W Product :-

$$\text{Bandwidth (B.W)} = f_2 - f_1$$

where  $f_2$  and  $f_1$  are the upper and lower half-power

frequencies of R-C Coupled transistor amplifier. Under normal operation  $f_2 \gg f_1$ . Therefore, B.W becomes

$$B.W \approx f_2 = \frac{1}{2\pi C_d (R_{c||h_{ie}})} \quad \text{--- (1)}$$

The product of B.W and gain (mid-frequency) of the amplifier is called gain-B.W product. For two stage R-C Coupled amplifier, the mid-frequency voltage gain of the first stage is given by

$$A_{VM1} = -\frac{h_{fe}}{h_{ie}} (R_{c||h_{ie}}) \quad \text{--- (2)}$$

and that of the second stage is given by

$$A_{VM2} = -\frac{h_{fe}}{h_{ie}} \cdot R_c \quad \text{--- (3)}$$

The over-all voltage gain is

$$A_{VM} = A_{VM1} \times A_{VM2} = \left(\frac{h_{fe}}{h_{ie}}\right)^2 (R_{c||h_{ie}}) \cdot R_c \quad \text{--- (4)}$$

The gain-B.W product =  $A_{VM} \times B.W$

$$= \frac{R_c}{2\pi C_d} \left(\frac{h_{fe}}{h_{ie}}\right)^2 = \text{Constant.}$$

$$\therefore \boxed{A_{VM} \propto \frac{1}{B.W}}$$