

Problems of Op-Amp.

1

Problem 1. An op-Amp has CMRR of 90dB. If its differential voltage gain is 3×10^4 . Calculate its common mode voltage gain.

Soln: $CMRR = \left| \frac{A_d}{A_c} \right|$

where A_d = difference mode voltage gain
and A_c = Common mode voltage gain of op-Amp.

In dB

$$CMRR = 20 \log_{10} \left| \frac{A_d}{A_c} \right|$$
$$= 20 \log_{10} \left| \frac{3 \times 10^4}{A_c} \right|$$

$$\Rightarrow 90 = 20 \log_{10} \left| \frac{3 \times 10^4}{A_c} \right|$$

$$\Rightarrow 9 = 2 \left[\log_{10} 3 \times 10^4 - \log_{10} A_c \right]$$

$$\Rightarrow \left[4 \log_{10} 10 + \log_{10} 3 - \log_{10} A_c \right] = \frac{9}{2}$$

$$\Rightarrow 4 + 0.477 - \log_{10} A_c = 4.5$$


$$\Rightarrow -\log_{10} A_c = 4.5 - 4.477 = 0.023$$

$$\Rightarrow +\log_{10} A_c = -0.023 \Rightarrow A_c = 10^{-0.023} = 0.9484$$

$\therefore A_c = 0.9484$

2

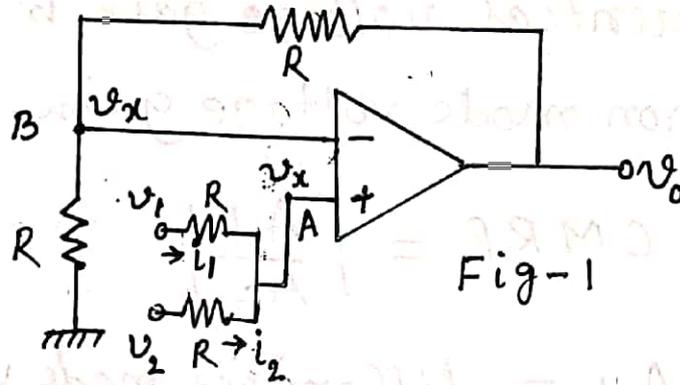Problem 2: Find the expression of the output voltage v_o of the following circuit of Fig-1.



Solⁿ: Let v_x be the potential at A. v_x is also the potential at B as per characteristic of an ideal op-Amp.

$$\therefore i_1 = \frac{v_1 - v_x}{R} \text{ and } i_2 = \frac{v_2 - v_x}{R}$$

$\therefore i = i_1 + i_2 = 0$ [no current will flow into the op-Amp because op-Amp has infinite input impedance or resistance]

$$\therefore \frac{v_1 - v_x}{R} + \frac{v_2 - v_x}{R} = 0$$

$$\Rightarrow \frac{v_1}{R} - \frac{v_x}{R} + \frac{v_2}{R} - \frac{v_x}{R} = 0$$

$$\Rightarrow -2v_x = -(v_1 + v_2) \Rightarrow v_x = \frac{1}{2}(v_1 + v_2)$$


On the basis of the concept of non-inverting amplifier, the output voltage is

$$v_o = (1 + R/R) v_x = 2 \times \frac{1}{2} (v_1 + v_2) = v_1 + v_2$$

$$\Rightarrow \boxed{v_o = v_1 + v_2}$$

Problem 3: Design a differential amplifier using op-Amp which will give an output voltage $v_o = 0.5v_1 - 2v_2$ where v_1 and v_2 are inputs of non-inverting and inverting terminals respectively

Soln

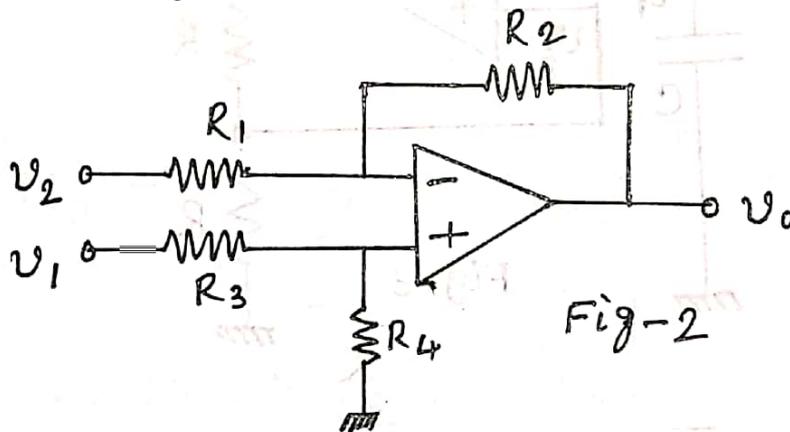

The expression of output v_o is given by

$$v_o = \left(\frac{R_1 + R_2}{R_3 + R_4} \right) \frac{R_4}{R_1} v_1 - \frac{R_2}{R_1} v_2$$

Let $R_2 = 2R_1$ and $R_3 = 5R_4$


4

$$\therefore v_0 = \left(\frac{R_1 + 2R_1}{R_4 + 5R_4} \right) \cdot \frac{R_4}{R_1} v_1 - \frac{2R_1}{R_1} v_2$$

$$\Rightarrow v_0 = \frac{3}{6} v_1 - 2v_2$$

$$\Rightarrow \boxed{v_0 = 0.5v_1 - 2v_2}$$

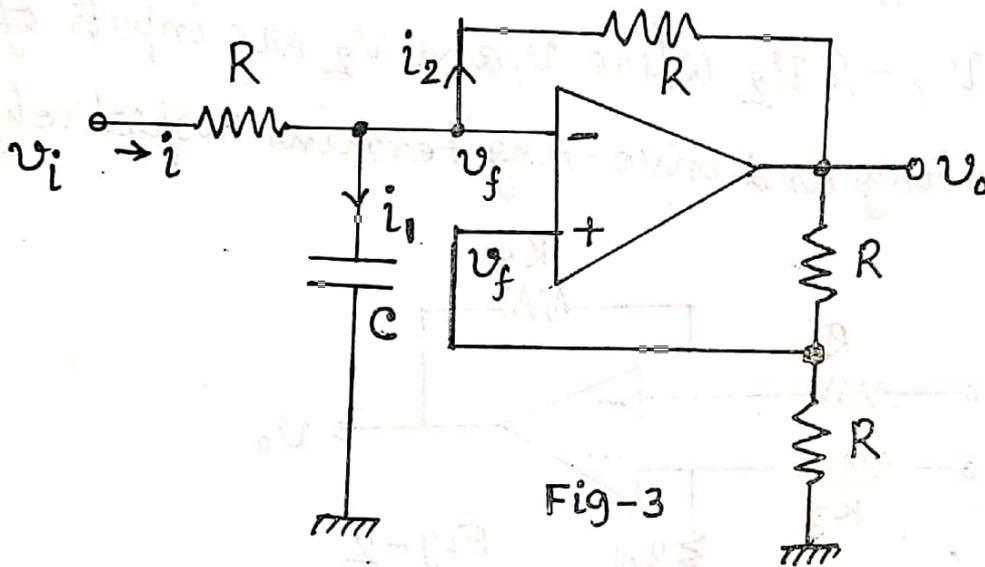Problem 4: Find the expression of v_0 of the circuit shown in Fig-3.



Solⁿ: On the basis of the circuit we can write

$$v_f = \frac{v_0 R}{R + R} = \frac{v_0}{2}$$

Again

$$i = i_1 + i_2$$

$$\therefore \frac{v_i - v_f}{R} = \frac{v_f - 0}{\frac{1}{sC}} + \frac{v_f - v_o}{R}$$

$$\Rightarrow \frac{v_i - v_f}{R} = \frac{v_f}{\frac{1}{sC}} + \frac{v_f - v_o}{R}$$

$$\Rightarrow v_i - v_f = sCR v_f + v_f - v_o$$

$$\Rightarrow v_i = sCR v_f + 2v_f - v_o$$

$$= (sCR + 2) v_f - v_o$$

$$= (sCR + 2) \frac{v_o}{2} - v_o$$

$$= v_o \left\{ \frac{sCR}{2} \right\}$$

$$\therefore v_o = \frac{2}{sCR} \cdot \frac{1}{s} v_i = \frac{2}{s^2 CR} \int v_i dt$$

$$\therefore v_o = \frac{2}{s^2 CR} \int v_i dt$$

$$\begin{aligned} \text{Let } r &= e^{j\omega t} \\ \therefore \frac{dr}{dt} &= j\omega e^{j\omega t} \\ &= j\omega r \end{aligned}$$

$$\therefore \frac{d}{dt} = j\omega = s$$

$$\therefore \frac{1}{s} = \int dt$$

Problem 5: An operational amplifier has an open-loop gain of 10^6 and open-loop upper cut-off frequency of 10 Hz . If the op-Amp is connected as an amplifier with a closed-loop gain of 100 , what will be the new upper cut-off frequency?

b

Solⁿ: Negative feedback amplifier always increases the upper cut-off frequency and hence increases the bandwidth of the amp.

The close-loop gain is $A_f = \frac{A}{1 + \beta A}$

Here $A = 10^6$ and $A_f = 100$ and upper cut-off frequency $f_2 = 10 \text{ Hz}$

$$\therefore (1 + \beta A) = \frac{A}{A_f} = \frac{10^6}{10^2} = 10^4$$

\therefore Upper cut-off frequency of close-loop amplifier is

$$f_{2f} = f_2 (1 + A\beta) = 10 \times 10^4 \text{ Hz} = 100 \text{ KHz}$$

Problem 6: Find the output v_o of the following circuit of Fig-4

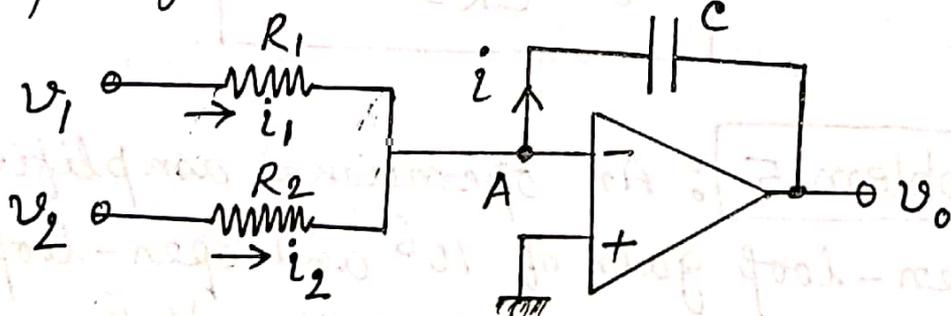


Fig-4: Summing integrator

7

Soln: The point A is at virtual ground so that $v_A = 0$ (op-Amp is used in inverting mode).

$$\text{Now } i_1 + i_2 = i$$


$$\Rightarrow \frac{v_1 - v_A}{R_1} + \frac{v_2 - v_A}{R_2} = \frac{v_A - v_o}{\frac{1}{sC}}$$

$$\Rightarrow \frac{v_1}{R_1} + \frac{v_2}{R_2} = -sC v_o$$

$$\Rightarrow v_o = -\frac{1}{sCR_1} v_1 - \frac{1}{sCR_2} v_2$$

$$\Rightarrow v_o = -\frac{1}{C} \int \left(\frac{v_1}{R_1} + \frac{v_2}{R_2} \right) dt$$

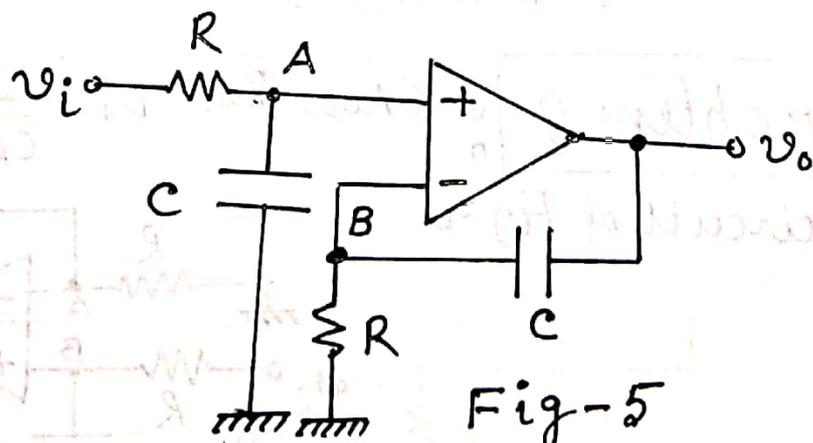Problem 7: Prove that the operational amplifier circuit as shown in fig-5 is an integrator. Assuming op-Amp is an ideal one.



8

Solⁿ: The voltage at the node A is

$$v_A = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} v_i = \frac{1}{1 + sCR} v_i \quad \dots (1)$$


As op-Amp is an ideal one $v_A = v_B = \frac{1}{1 + sCR} v_i$

For non-inverting mode of op-Amp, the output voltage is

$$\begin{aligned} v_o &= \left(1 + \frac{sC}{R}\right) v_A \\ &= \frac{1 + sCR}{sCR} v_A \\ &= \frac{(1 + sCR)}{sCR} \cdot \frac{v_i}{(1 + sCR)} \quad (\text{using (1)}) \end{aligned}$$

$$= \frac{v_i}{sCR} = \frac{1}{CR} \int v_i(t) dt \quad \text{as } \frac{1}{s} = \int dt$$

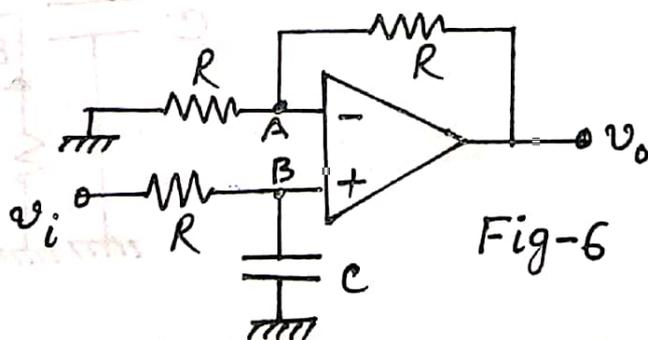Problem 8: Show that $v_o = \frac{2}{CR} \int v_i dt$ of the circuit of Fig-6



Soln: $v_B = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} v_i = \frac{1}{1 + sCR} v_i$

We assume the op-Amp is an ideal one then

$$v_A = v_B = \frac{1}{1 + sCR} v_i$$

Considering the non-inverting op-Amp we can write the output voltage


$$v_o = \left(1 + \frac{R}{R}\right) v_B = 2 v_B$$

$$v_o = \frac{2}{1 + sCR} v_i$$

assuming $sCR \gg 1$

$$v_o = \frac{2}{sCR} \cdot \frac{1}{s} v_i = \frac{2}{s^2 CR} \int v_i dt$$

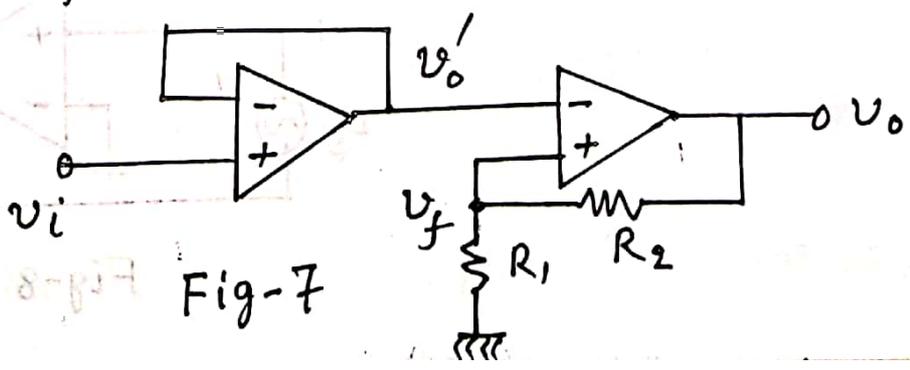Problem 9 Calculate the output voltage v_o of the circuit of Fig-7



10.

Solⁿ :- Since the 1st stage is a unity gain buffer so that $v_o' = v_i$

$$\text{Now } v_f = \frac{v_o R_1}{R_1 + R_2}$$


For an ideal op-Amp $v_f = v_o' = v_i$

$$\therefore \frac{v_o R_1}{R_1 + R_2} = v_i$$

$$\Rightarrow v_o = \left(\frac{R_1 + R_2}{R_1} \right) v_i = \left(1 + \frac{R_2}{R_1} \right) v_i$$

$$\therefore \boxed{v_o = \left(1 + \frac{R_2}{R_1} \right) v_i}$$

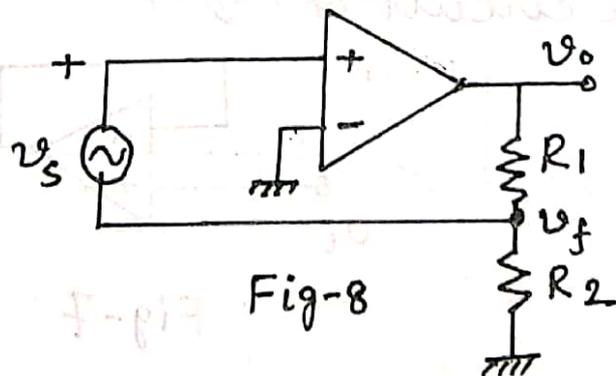Problem 10 :- A feedback amplifier circuit is shown in Fig-8 with the gain of amplifier $A = 100 \angle 180^\circ$, $R_1 = 10 \text{ k}\Omega$ and $R_2 = 150 \text{ k}\Omega$. Calculate output voltage and source voltage when input voltage of amplifier is $1 \angle 0^\circ$



Soln: The given circuit configuration is voltage series feedback. The feedback voltage

$$v_f = \frac{R_2}{R_1 + R_2} v_o = \frac{150}{160} v_o = \beta v_o$$

The feedback path gain is $\beta = \frac{150}{160}$

The overall voltage gain

$$\begin{aligned} A_f = \frac{v_o}{v_s} &= \frac{A}{1 + \beta A} = \frac{100 \angle 180^\circ}{1 + \frac{150}{160} \times 100 \angle 180^\circ} \\ &= \frac{-100}{1 + \frac{150}{160} \times (-100)} \\ &= 1.078 \end{aligned}$$

$$\text{Hence } v_o = 1.078 v_s$$

The input voltage of the basic amplifier is

$$\begin{aligned} v_i &= v_s - v_f = v_s - \beta v_o \\ &= v_s - \frac{150}{160} \times 1.078 v_s \\ &= -0.010625 v_s \end{aligned}$$

As $v_i = 1 \angle 0^\circ$, the source voltage is

$$v_s = -\frac{v_i}{0.010625} = -\frac{1 \angle 0^\circ}{0.010625} = -94.11 \angle 0^\circ$$

$$\therefore v_o = 1.078 v_s = 1.078 \times (-94.11 \angle 0^\circ) = -101.45 \angle 0^\circ$$

Problem 11: An amplifier has a gain of -100 and feedback ratio is $\beta = -0.05$. Determine
 (1) The close-loop voltage gain (2) The amount of feedback in dB (3) The feedback factor and
 (4) feedback voltage. Assume $v_s = 50 \text{ mV}$

Solⁿ: Given $A = -100$, $\beta = -0.05$

$$(1) \text{ Close-loop voltage gain } A_f = \frac{A}{1 + \beta A} = \frac{-100}{1 + (-0.05) \times (-100)}$$

$$= -16.67$$

$$(2) \text{ Amount of feedback in dB} = 20 \log_{10} \left| \frac{A_f}{A} \right|$$

$$= 20 \log_{10} \left| \frac{-16.67}{-100} \right|$$

$$= 20 \left[\log_{10} 16.67 - \log_{10} 10^2 \right]$$

$$= 20 \left[1.223 - 2 \right]$$

$$= -15.56 \text{ dB}$$

(3) The feedback factor or feedback gain

$$\beta A = (-100) \times (-0.05) = 5$$

$$(4) v_f = \beta v_o = \beta A_f v_s = (-0.05) \times (-16.67) \times 50 \text{ mV} = 41.675 \text{ mV}$$

Problem 12 : In a voltage-series feedback amplifier $A = 400$, $R_i = 2\text{K}\Omega$, $R_o = 100\text{K}\Omega$ and $\beta = 0.1$, determine overall gain, input resistance and output resistance of the feedback amplifier.

Soln : Given $A = 400$, $R_i = 2\text{K}\Omega$, $R_o = 100\text{K}\Omega$ and $\beta = 0.1$.

In voltage-series feedback amplifier

$$\text{Overall gain is } A_f = \frac{A}{1+A\beta} = \frac{400}{1+0.1 \times 400} = 9.756 \quad \text{---(1)}$$

$$\begin{aligned} \text{Input resistance } R_{if} &= R_i(1+A\beta) \quad \text{---(2)} \\ &= 2 \times 10^3 \times (1+0.1 \times 400) \\ &= 82\text{K}\Omega \end{aligned}$$

$$\begin{aligned} \text{Output resistance } R_{of} &= \frac{R_o}{1+A\beta} = \frac{100 \times 10^3}{1+0.1 \times 400} \\ &= 2.439\text{K}\Omega \quad \text{---(3)} \end{aligned}$$

All three expressions for A_f , R_{if} and R_{of} are also applicable to current-series feedback amplifiers.

They are $A_f = \frac{A}{1+A\beta}$; $R_{if} = R_i(1+A\beta)$ and

$$R_{of} = \frac{R_o}{1+A\beta}.$$

14

Problem 13: Determine overall gain,

input impedance and output impedance of a voltage-shunt feedback amplifier.

Assume the following parameters of feedback amplifier. open-loop gain $A = -1000$, input resistance $R_i = 10\text{ k}\Omega$, output resistance $R_o = 20\text{ k}\Omega$ and $\beta = -0.1$.

Soln:

$$A_f = \frac{A}{1+A\beta} = \frac{-1000}{1+(-0.1)\times(-1000)} = -9.90$$

$$R_{if} = \frac{R_i}{1+A\beta} = \frac{10\text{ k}\Omega}{1+(-0.1)\times(-1000)} = 99\Omega$$

$$R_{of} = \frac{R_o}{1+A\beta} = \frac{20 \times 10^3}{1+(-0.1)\times(-1000)} = 198\Omega$$

Problem 14: Compute the input and output impedances for an amplifier in a current-shunt feedback configuration with $A = 500$, $R_i = 1000\Omega$, $R_o = 5000\Omega$ and $\beta = 0.075$

Solⁿ: Given $A = 500$, $R_i = 1000 \Omega$, $R_o = 5000 \Omega$
and $\beta = 0.075$


In current-shunt configuration feedback amplifier

$$R_{if} = \frac{R_i}{1 + A\beta} = \frac{1000 \Omega}{1 + 0.075 \times 500} = 25.97 \Omega$$

$$R_{of} = R_o (1 + A\beta) = 5000 \times (1 + 0.075 \times 500) \Omega = 192.5 \text{ K}\Omega.$$

Voltage Series Negative Feedback Amplifier:

Non-inverting op-Amp:

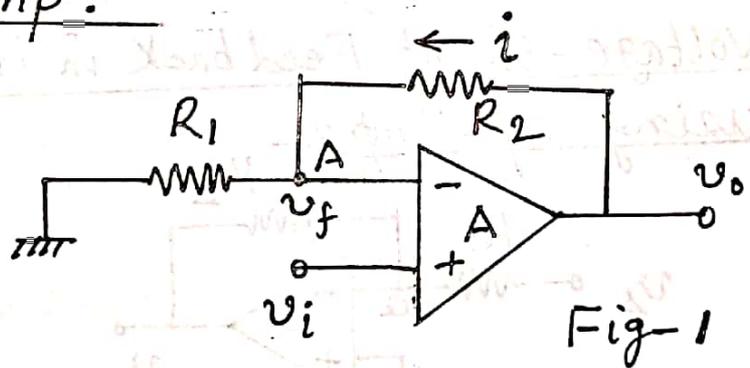

From Fig-1

$$i = \frac{v_o - v_f}{R_2} = \frac{v_f}{R_1}$$

$$\Rightarrow v_f = \frac{R_1}{R_1 + R_2} v_o = \beta v_o$$

where $\beta = \frac{v_f}{v_o}$ = feedback factor for voltage-series feedback

Let A and $(v_i - v_f)$ be the open-loop voltage gain and differential input to basic amplifier respectively.

16

$$\therefore v_o = A(v_i - v_f) = A(v_i - \beta v_o)$$

$$\Rightarrow v_o(1 + A\beta) = Av_i$$

Therefore close-loop voltage gain of the voltage-series amplifier is

$$A_f = \frac{v_o}{v_i} = \frac{A}{1 + A\beta} = \frac{1}{\frac{1}{A} + \beta}$$

In the limit $A \rightarrow \infty$; $A_f = \frac{1}{\beta} = \frac{R_1 + R_2}{R_1}$

$$\therefore A_f = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1}$$

Voltage-Shunt Feedback in inverting amplifier using op-Amp :-

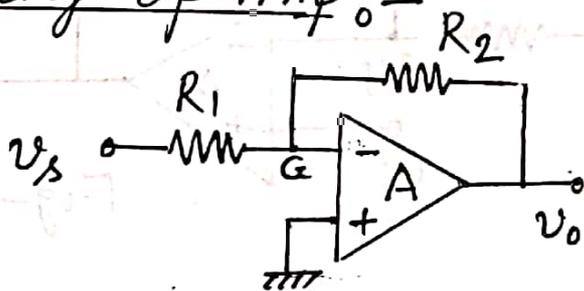


Fig-2

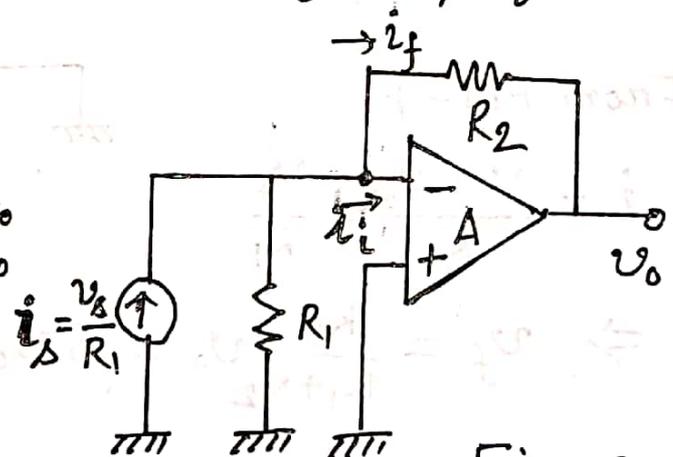


Fig-2(a)

Fig-2 shows the voltage-shunt feedback. Its equivalent circuit is shown in Fig-2(a)

The gain of the amplifier

$$A = \frac{v_o}{i_i}; \quad A \rightarrow \infty \text{ as } i_i \rightarrow 0$$

The feedback gain is $\beta = \frac{i_f}{v_o} = -\frac{1}{R_2}$

The block-diagram representation of Fig-2(a) is shown in Fig-2(b).

The overall loop gain is

$$A_f = \frac{v_o}{i_s} =$$

$$= \frac{A}{1 + A\beta}$$

$$= \frac{A}{1 - A/R_2}$$

$$= \frac{1}{\frac{1}{A} - \frac{1}{R_2}} = -R_2$$

$$\text{As } A \rightarrow \infty \text{ and } i_i \rightarrow 0$$

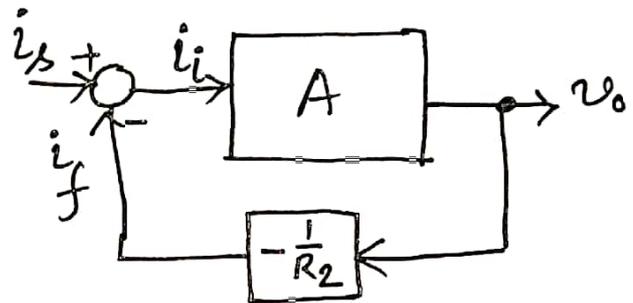


Fig-2(b)

The voltage gain (closed-loop)

$$A_{vf} = \frac{v_o}{v_s} = \frac{v_o}{i_s} \cdot \frac{i_s}{v_s} = -\frac{R_2}{R_1} \text{ as } \frac{v_o}{i_s} = -R_f$$

$$\text{and } \frac{i_s}{v_s} = \frac{1}{R_1}$$

Feedback Connection types

①

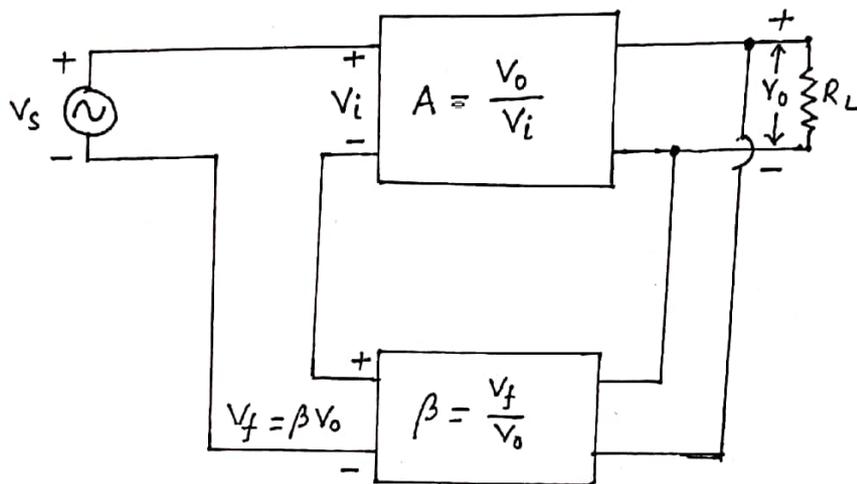


Fig-1 : Voltage-Series feedback : $A_f = \frac{V_o}{V_s} = \frac{A}{1+A\beta}$

②

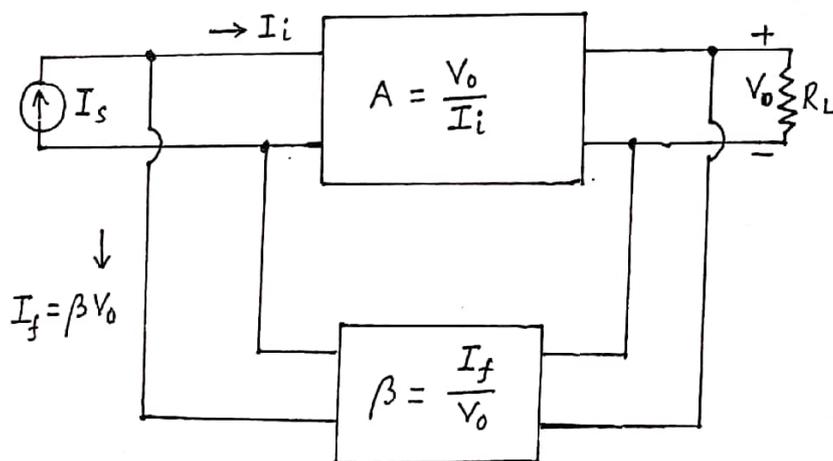


Fig-2 : Voltage-Shunt feedback : $A_f = \frac{V_o}{I_s} = \frac{A}{1+A\beta}$

(3)

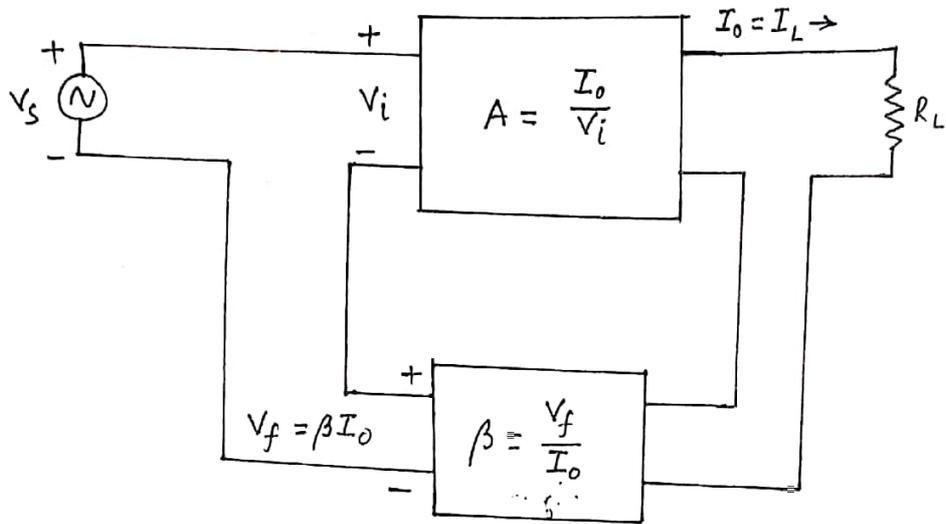


Fig-3: Current-Series feedback: $A_f = \frac{I_o}{V_s}$

(4)

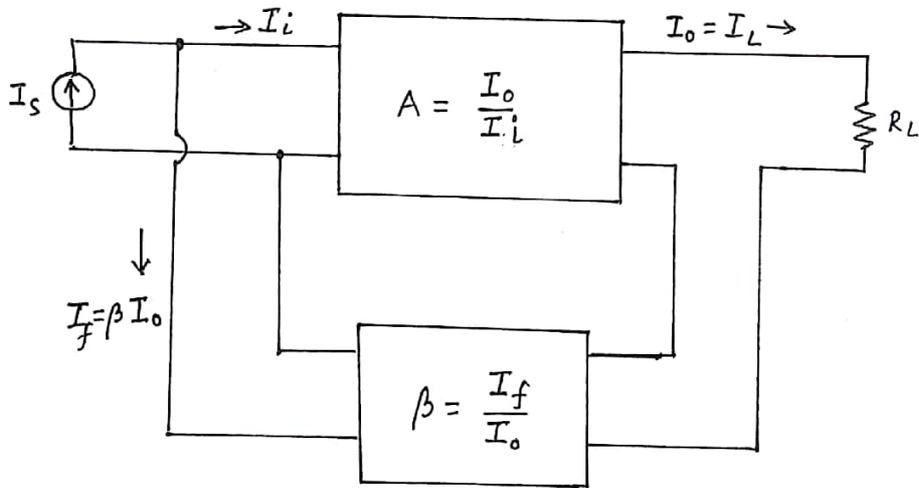


Fig-4: Current-Shunt feedback: $A_f = \frac{I_o}{I_s}$